
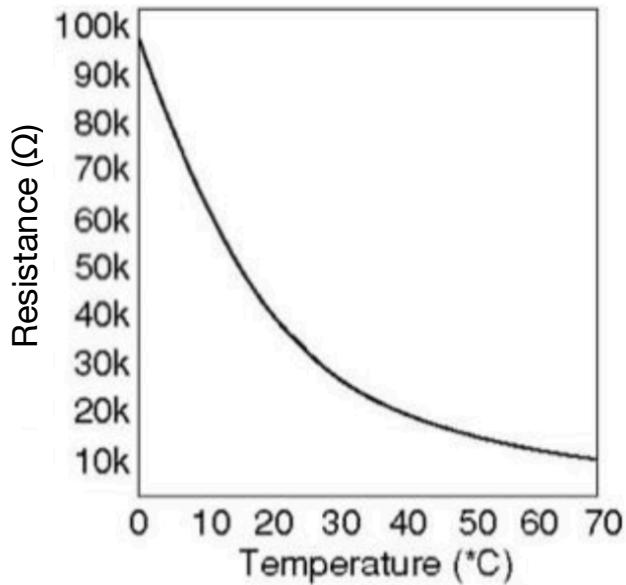


Follow the homework guidelines on the course webpage to answer the following.

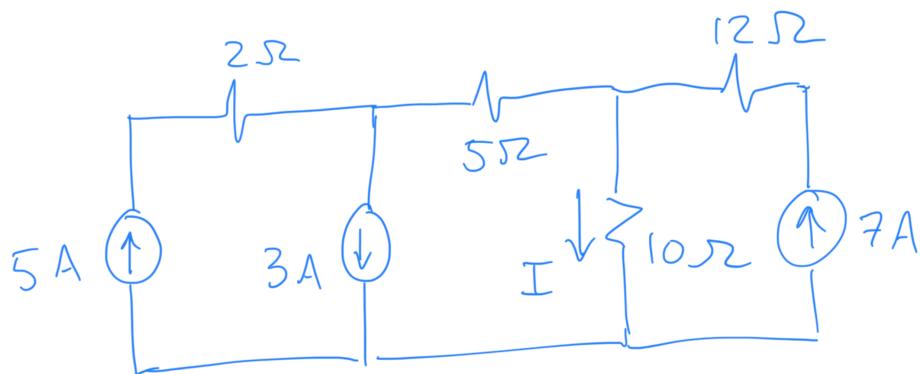1. The figure shown below shows the relationship between resistance and temperature for a thermistor. Estimate the coefficient  $\beta$ .



2. What voltage battery is needed to produce 500 milliAmps of current in a circuit with  $24 \Omega$  of resistance?
3. Find current  $I$  in the circuit shown below.



4. An unknown resistor,  $R_2$ , is connected in series with two other resistors ( $R_1 = 20 \Omega$  and  $R_3 = 25 \Omega$ ) and a 15 V battery. You know the current in the loop is 200 mA.

- (a) What is the total resistance of the circuit?
- (b) What is the resistance of  $R_2$ ?
- (c) What is the current through each resistor?
- (d) What is the voltage drop across each resistor?

5. Find the intensity,  $I$ , of light transmitted through a sample if the absorbance is 0.21 and the incident light,  $I_0$ , is 1.0.